

## **EE561: Power Electronics Laboratory**

### **Experiment 1: Simulation of Buck Converter using MATLAB/SIMULINK**

**Objective:** The objective of this experiment is to familiarize the student with MATLAB/SIMULINK and important simulation settings. For this a buck converter with the following parameters has to be designed and simulated.

#### **Parameters of the Buck Converter**

Input voltage: 24 V

Output voltage: 12 V

Output power: 100 W

Switching frequency: 100 kHz

Ripple in inductor current: 25%

Ripple in output voltage: 0.1%

#### **Report**

The report should contain the following information

Circuit diagram and theoretical waveforms of buck converter

Design procedure and final design parameters obtained

Snapshot of the simulated circuit

Simulation results obtained: Input voltage, Output voltage, switching signal, inductor current, voltage across switch, voltage across diode

Snapshot of the simulation configuration parameters

**Note:** In Simulink, the circuit has to be simulated using a fixed time-step solver